
Report for Laboratory Three: RC Circuit Response

Austin Piper

Alex Blakley

Irfan Ahmed

*Department of Mechanical Engineering, Saint Martin's University
ME/EE 316—Mechatronics & Measurements Laboratory*

October 7, 2020

Abstract. The purpose of this lab was to view and measure the response of the voltage across a capacitor in a RC circuit. After building the circuit on a breadboard we sent 1 volt across the completed circuit and we used the myRIO microcontroller in order to record the results. The output voltage and resulting graphs can be used to find the time constant.

1 Introduction

There are many variations of circuits used in the world of electronics in order to accomplish and power useful machines. The common RC circuit is used in devices like pacemakers, noise cancelling products, and timing circuits. These types of circuits are used because they can filter signals, blocking some and allowing others to pass through and therefore they are effective in their usage.

In this lab, we built a basic RC circuit on a breadboard with a single $100\text{ k}\Omega$ resistor and a $10\text{ }\mu\text{F}$ capacitor. We hooked up the myRIO to the breadboard and, with the full circuit completed and grounded using jumper wires, we applied a DC voltage across the capacitor and the measurements were taken of both the source voltage and output voltage. The advantage of using the myRIO is that we could pair this technology with the LabVIEW program in order to have a graph drafted, in real time, of both of the data streams we require in order to deepen our understanding of how the RC circuit reacts to a constant voltage over time.

2 Materials and Methods

This experiment started with the building of a circuit that had a $100\text{ k}\Omega$ resistor and a $10\text{ }\mu\text{F}$ capacitor in series using a breadboard and jumper wires. Using a multimeter, both the capacitor and resistor were measured in order to ensure they, indeed, had the desired value of capacitance and resistance we needed for the experiment. After the myRIO was connected to our circuit we then began setting up the LabVIEW program in order to both control the source voltage supplied across the capacitor and to measure the output voltage over time. Using LabVIEW, we were able to grab the data and create a graph that showed both of the aforementioned voltages after about 6 time constants ($6RC$).

3 Results

By conducting a circuit analysis of our circuit seen in [Figure 1](#), we found the equation for voltage across the capacitor. Using the that equation we were able to derive the equation for τ . Once we had our equations we used the data collected

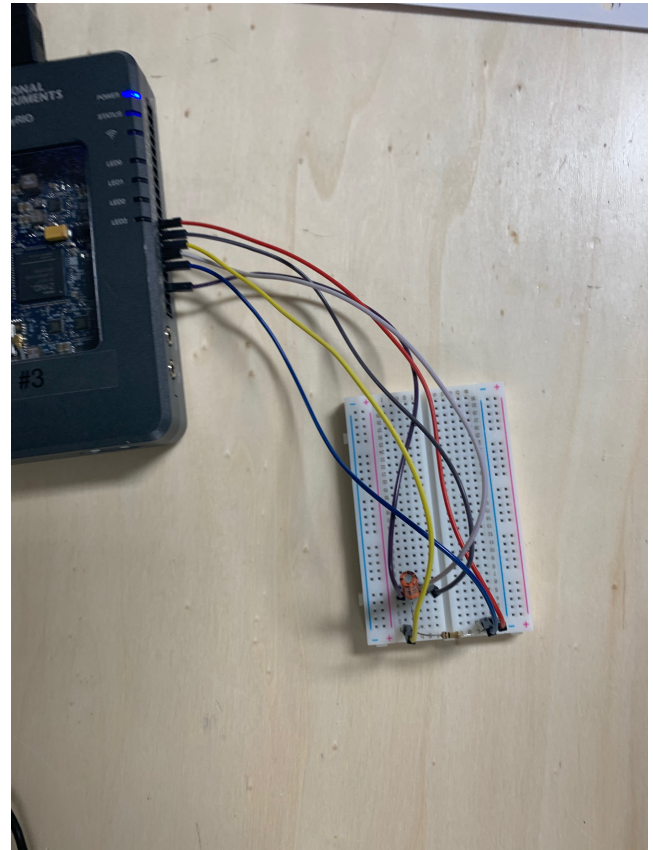


Figure 1: RC Circuit

from LABVIEW and plotted our V_c in [Figure 4](#). On the same plot we compared the V_s and V_o vs time [Figure 2](#) then after linearizing our data we were able to find out time constant value $\tau = 1.01325$. [Figure 3](#)

4 Discussion

This lab showed that the response of a RC circuit by measuring the time response of the voltage across a $10\mu\text{F}$ capacitor. We applied a voltage source and measured the output voltage using the myRIO. Observing the data showed us that our capacitor was gaining voltage over time. Our time constant was larger than one therefore it took a fairly long time

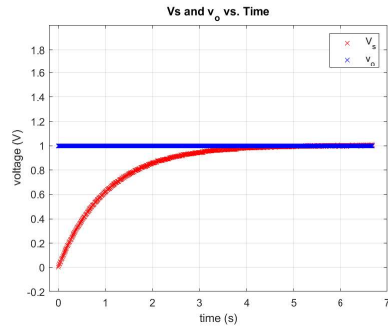


Figure 2: Voltage vs. Time

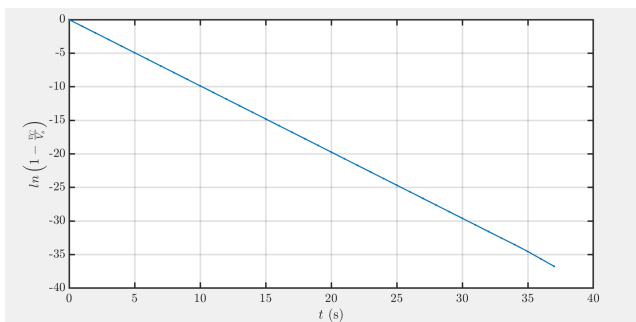
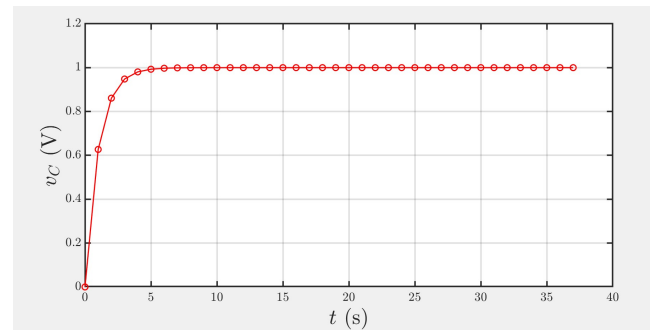


Figure 3: Linearized data

Figure 4: v_c vs. Time

	R (kΩ)	C (μF)
Nominal	100	10
Measured	99.4	10.2

Table 1: Multimeter Measurements

methods section. Austin applied the photos and the table. He also wrote the results and discussion sections. Irfan made the circuit diagram and did the circuit analysis.

to charge the capacitor.

5 Equations

$$V_c(t) = V_s \left(1 - e^{-\frac{t}{\tau}} \right)$$

$$\tau = \frac{-t}{\ln \left(1 - \frac{V_c(t)}{V_s(t)} \right)}$$

6 Author Contributions

Alex created the voltage versus time graph. He also wrote the abstract, the introduction, and wrote the materials and